

Rx DFE (1-tap)

12 Gbps


Muhammad Aldacher

Outline


1. Design Implementation
2. Tests & Simulations
 - a) Pulse Response
 - b) Frequency response (DFE loop open)
 - c) Eye Diagrams (DFE loop closed)
3. Summary

DFE Design Implementation

Concept

 

Implementation

 

Tests & Simulations


Design Parameters

Parameter	Value
Data Rate	12 Gb/s
VDD (for CTLE & DFE)	1.2 V
Input $V_{\text{SWING (PK2PK)}}$ [From TX side]	0.4 V
Input V_{CM} [From TX side]	0.75 V
Channel	14-inch FR4
Output V_{CM}	0.6 V

CTLE design used is based on this project:

<https://github.com/muhammaddacher/SERDES-Design-of-RX-Continuous-time-linear-equalizer>


Channel = 14 x 1-inch FR4 section

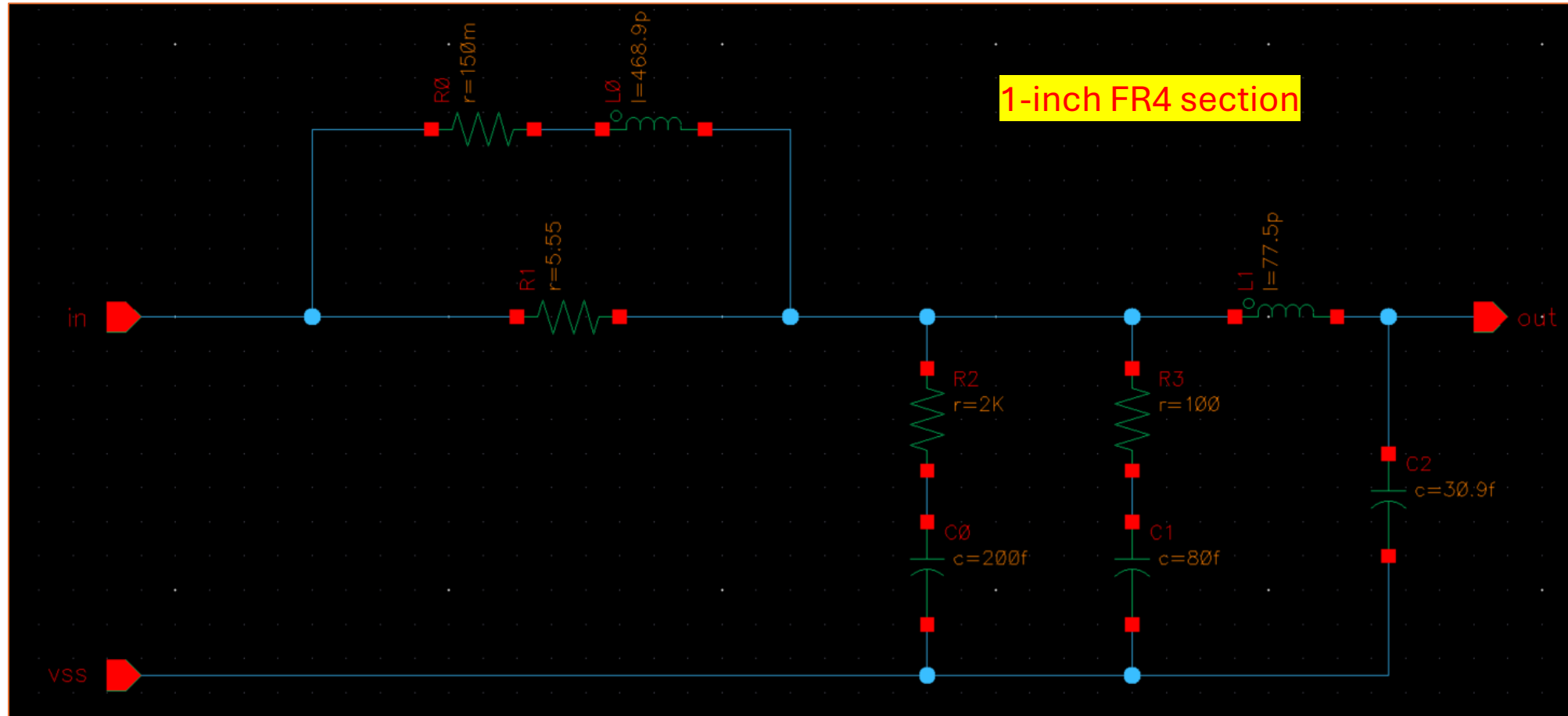

a) Pulse Response

This test is to see how much the post-cursors' values are compared to the main cursor value

a) Pulse Response: Testbench

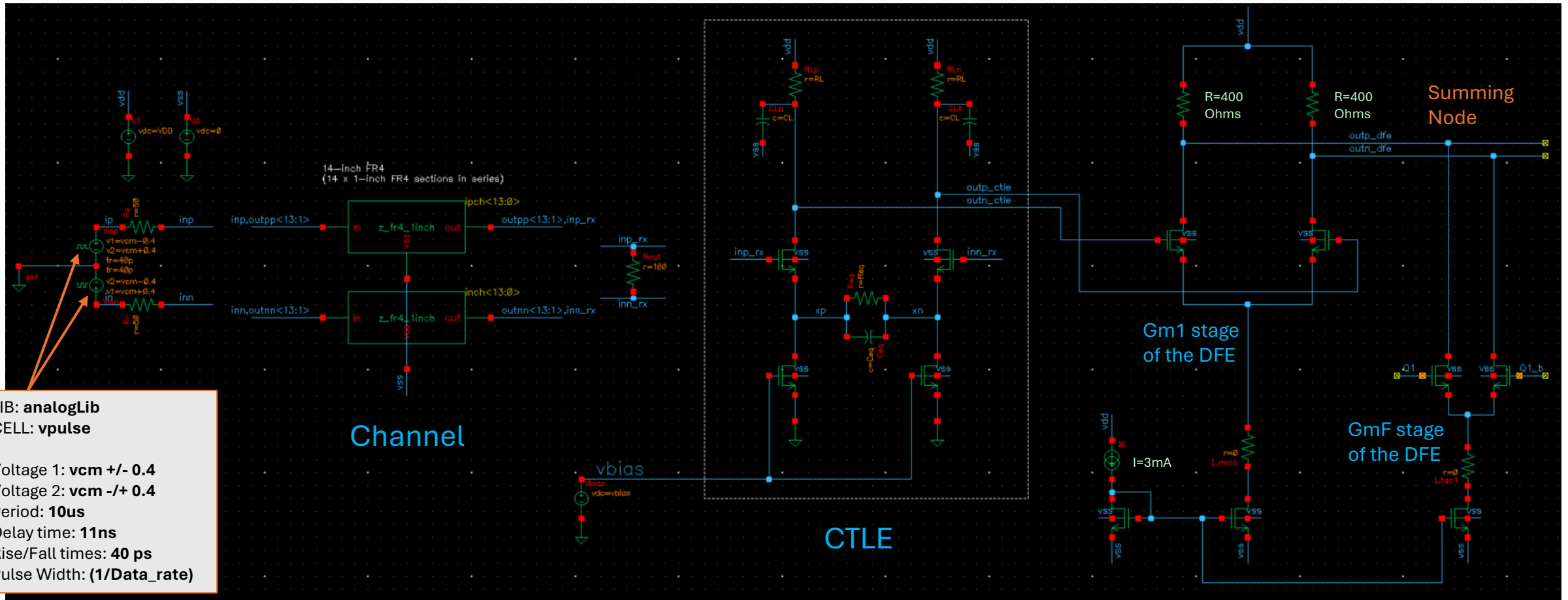

a) Pulse Response: Setup

Name	Value
Filter	
Tests	
Transient	
Simulator	spectre
Analyses	
tran	0 VAR("sim_time")
Click to add analysis	
Design Variables	
Click to add test	
Global Variables	
sim_time	15n
VDD	1.2
Data_rate	12G
vcm	0.75
vbias	600m
RL	400
CL	50f
Req	1K
Ceq	250f

CTLE
Parameters

Choosing Analyses - ADE Assembler

Analysis

☒ tran ☐ dc ☐ ac
☐ noise ☐ xfb ☐ sens
☐ dcmatch ☐ acmatch ☐ stb
☐ pz ☐ lf ☐ sp
☐ envlp ☐ pss ☐ pac
☐ pstb ☐ pnoise ☐ pxf
☐ psp ☐ qpss ☐ qpac
☐ qpnoise ☐ qpfb ☐ qpss
☐ hb ☐ hbac ☐ hbstb
☐ hbnoise ☐ hbfb ☐ hbfb

Transient Analysis

Stop Time: VAR("sim_time")

Accuracy Defaults (errpreset)

☐ Transient Noise

Dynamic Parameter ☐

☐ HV_solution
Enabled ☒

Options...

OK Cancel Defaults Apply Help

a) Pulse Response: Measurements

Name	Type	Details	EvalType
Filter	Filter	Filter	Filter
	signal	/vcm	point
	signal	/ip	point
	signal	/in	point
	signal	/inp	point
	signal	/inn	point
	signal	/inp_rx	point
	signal	/inn_rx	point
	signal	/outp_ctle	point
	signal	/outn_ctle	point
	signal	/outp_dfe	point
	signal	/outn_dfe	point
*** PK2PK ***	expr		point
Vchin_pk2pk	expr	$(VT("/inp") - VT("/inn"))$	point
Vchout_pk2pk	expr	$((VT("/inp_rx") - VT("/inn_rx")) + 0.4)$	point
Vctleout_pk2pk	expr	$(VT("/outp_ctle") - VT("/outn_ctle"))$	point
Vdfeout_pk2pk	expr	$(VT("/outp_dfe") - VT("/outn_dfe"))$	point
** Main Cursor **	expr		point
Data_rate	expr	$VAR("Data_rate")$	point
UI	expr	$(1 / Data_rate)$	point
t_cursor_main	expr	$xmax(Vchout_pk2pk)$	point
cursor_main	expr	$value(Vchout_pk2pk \ t_cursor_main)$	point
** Post & Pre Cursors **	expr		point
t_cursor_pre_1	expr	$(t_cursor_main - UI)$	point
t_cursor_post_1	expr	$(t_cursor_main + UI)$	point
t_cursor_post_2	expr	$(t_cursor_main + (2 * UI))$	point
cursor_pre_1	expr	$value(Vchout_pk2pk \ t_cursor_pre_1)$	point
cursor_post_1	expr	$value(Vchout_pk2pk \ t_cursor_post_1)$	point
cursor_post_2	expr	$value(Vchout_pk2pk \ t_cursor_post_2)$	point
percent_pre_1	expr	$((cursor_pre_1 / cursor_main) * 100)$	point
percent_post_1	expr	$((cursor_post_1 / cursor_main) * 100)$	point
percent_post_2	expr	$((cursor_post_2 / cursor_main) * 100)$	point

← Pk2Pk Output of Channel (We add Vswing(PK2PK) to shift the whole curve to above 0)

← Pk2Pk Output of CTLE

← Pk2Pk Output of DFE Gm1 stage (Summing Node)

← Time of Main Cursor

← Value of Main Cursor

← Times of Pre & Post Cursors

← Values of Pre & Post Cursors


← Percentages of Pre & Post Cursors (with respect to the main cursor)

Note:

DFE is used to cancel Post-Cursors only

a) Pulse Response: Waveforms


	Channel Outputs			
	Pre-Cursor 1	Main-Cursor	Post-Cursor 1	Post-Cursor 2
Time	11.07866 ns	11.162 ns	11.24533 ns	11.32866 ns
Voltage	220.81 mV	483.12 mV	235.72 mV	115.31 mV
Percentage (compared to Main Cursor)	46 %	100 %	48.8 %	23.9 %

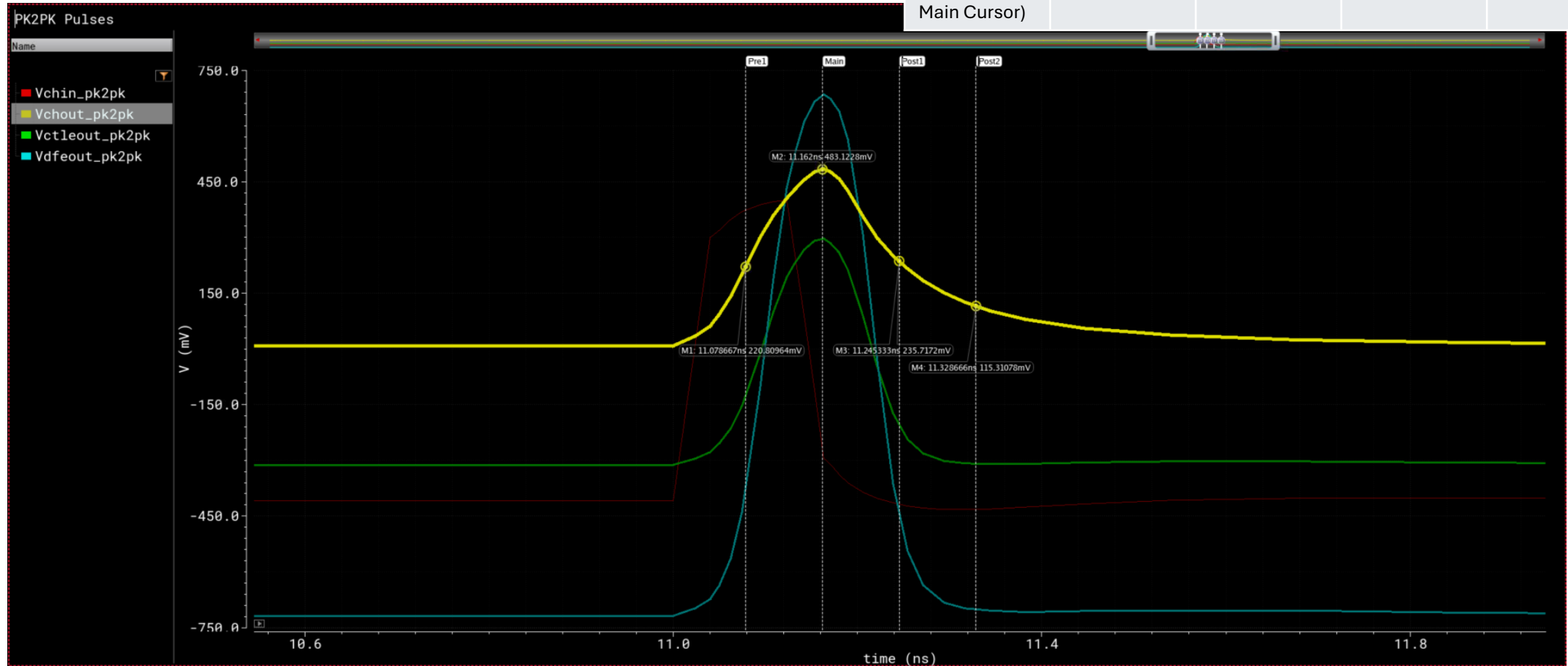

b) Frequency Response

This test is to design the Gm1 stage of the DFE.
(DFE's loop is open)

b) Frequency Response: Testbench

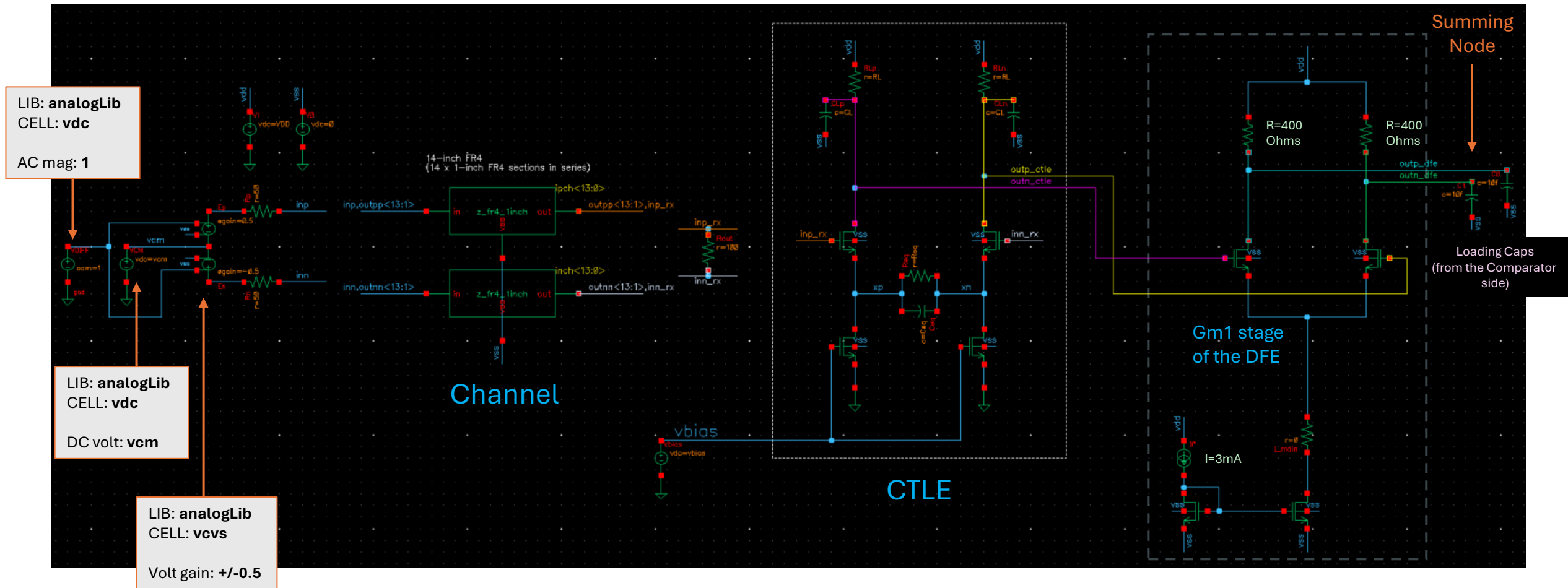

b) Frequency Response: Setup

The screenshot shows a simulation setup window with a tree view on the left and a table of global variables. The 'AC' analysis is selected under 'Analyses'. The 'ac' analysis is configured with '1M 15G 100 Logarithmic Points Per Decade Start-Stop'. A red box highlights the 'ac' analysis entry. A red arrow points from this box to the 'AC Analysis' dialog box on the right. A bracket on the right side of the global variables table groups the last seven variables (VDD, Data_rate, vcm, vbias, RL, CL, Req, Ceq) under the label 'CTLE Parameters'.

Name	Value
VDD	1.2
Data_rate	12G
vcm	0.75
vbias	600m
RL	400
CL	50f
Req	1K
Ceq	250f

CTLE Parameters

The 'AC Analysis' dialog box is shown with the following settings:

- Sweep Variable:** ☒ Frequency, ☐ Design Variable, ☐ Temperature, ☐ Component Parameter, ☐ Model Parameter, ☐ None
- Sweep Range:** ☒ Start-Stop, ☐ Center-Span. Start: 1M, Stop: 15G
- Sweep Type:** ☒ Logarithmic, ☐ Points Per Decade, ☐ Number of Steps. Value: 100
- Add Specific Point:** ☐
- Add Points By File:** ☐
- Specialized Analyses:** None
- Enabled:** ☒

Buttons: OK, Cancel, Defaults, Apply, Help, Options...

b) Frequency Response: Measurements

Name	Type	Details	EvalType
Hf_gm1	expr	$\text{dB20}(((\text{VF}("/\text{outp_dfe}") - \text{VF}("/\text{outn_dfe}")) / (\text{VF}("/\text{outp_ctle}") - \text{VF}("/\text{outn_ctle}"))))$	point
Hf_ch	expr	$\text{dB20}((\text{VF}("/\text{inp_rx}") - \text{VF}("/\text{inn_rx}")))$	point
Hf_ctle	expr	$\text{dB20}((\text{VF}("/\text{outp_ctle}") - \text{VF}("/\text{outn_ctle}")))$	point
Hf_dfe	expr	$\text{dB20}((\text{VF}("/\text{outp_dfe}") - \text{VF}("/\text{outn_dfe}")))$	point
Hf_at_DC	expr	$\text{value}(\text{Hf_dfe } 0)$	point
Hf_at_Nyq	expr	$\text{value}(\text{Hf_dfe } (\text{VAR}("Data_rate") / 2))$	point

Gain of DFE Gm1 stage

Gain from inputs to Channel outputs


Gain from inputs to CTLE outputs

Gain from inputs to DFE Gm1 outputs


Total Gain (Loss) at DC

Total Gain (Loss) at Nyquist (6 GHz)

b) Frequency Response: Results

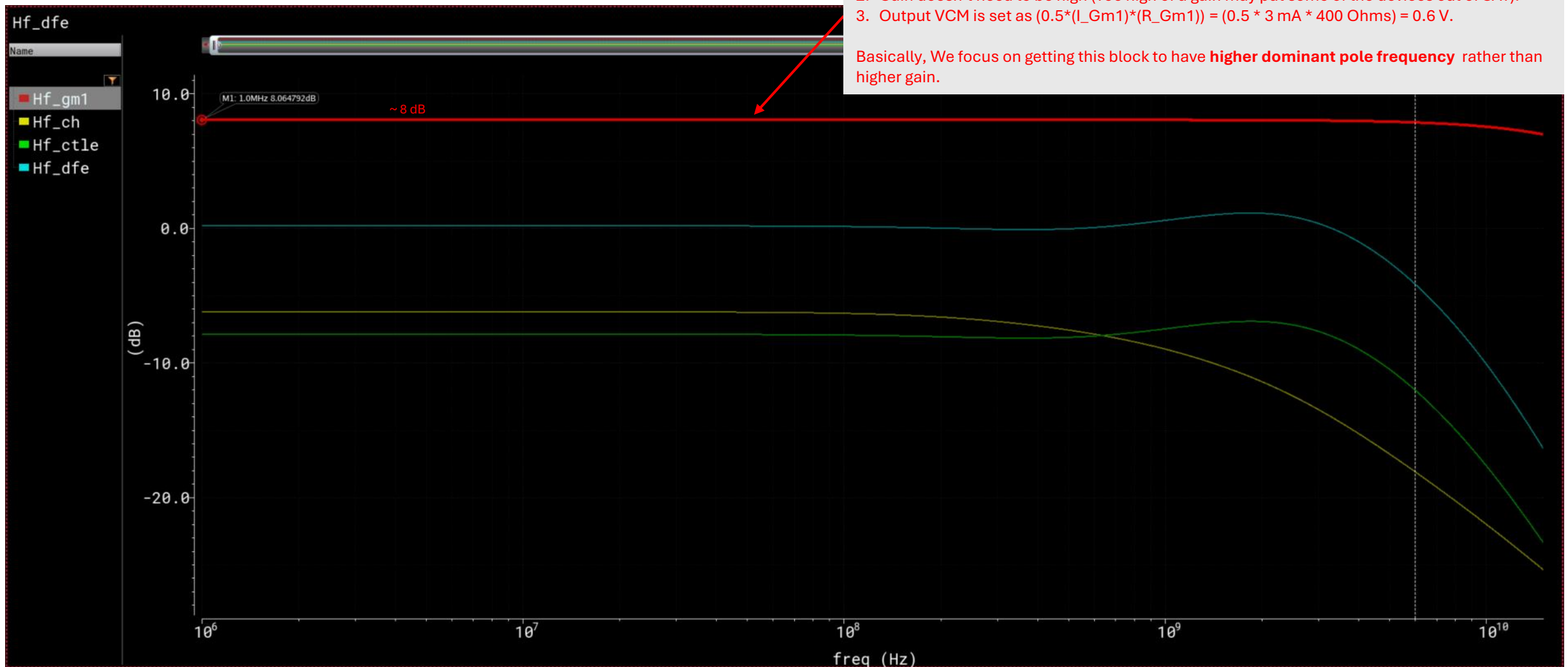

b) Frequency Response: Results

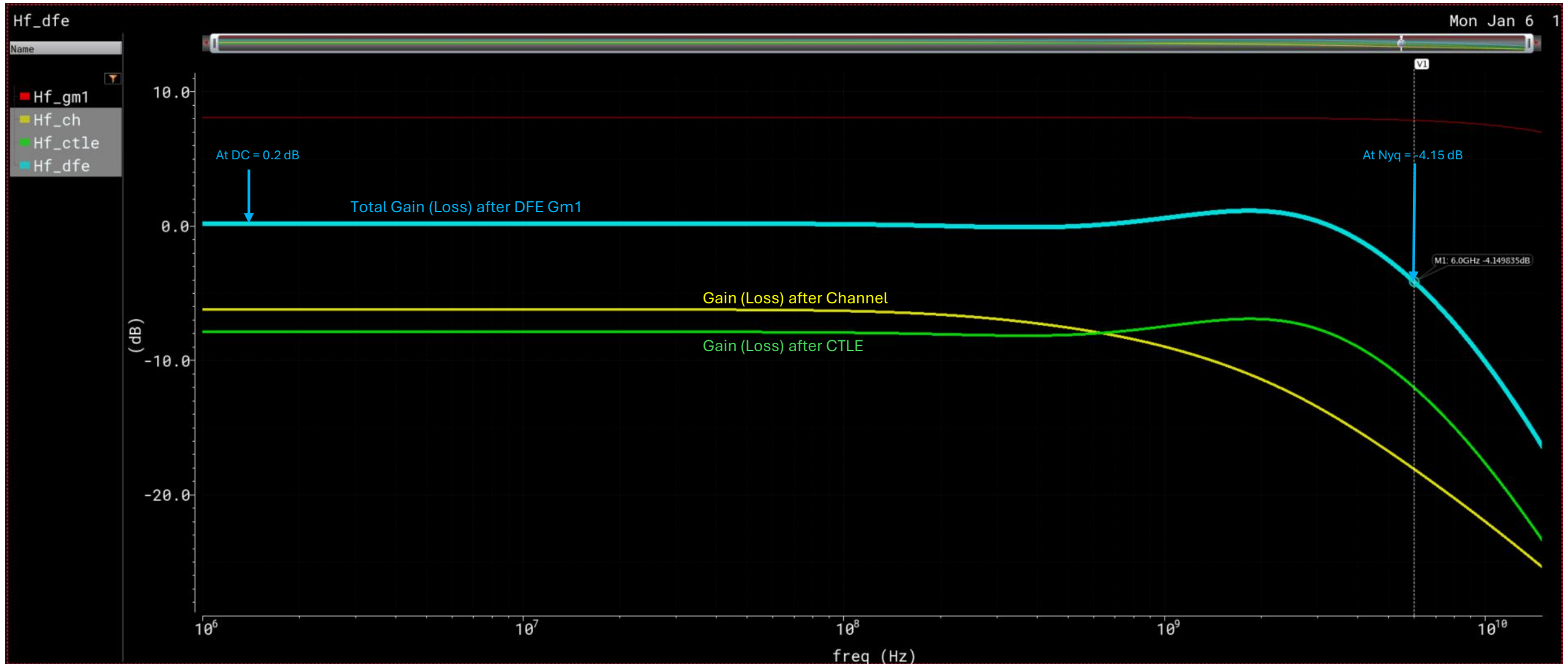

c) Eye Diagrams

This test is to check the performance with
different values for DFE taps


(DFE's loop is closed + Only using 1 tap)

c) Eye Diagrams: Testbench


LIB: analogLib
CELL: vprbs

Zero value: $v_{cm} \pm 0.4$
One value: $v_{cm} \mp 0.4$
Bit period: **83.33ps**
(1/12G)

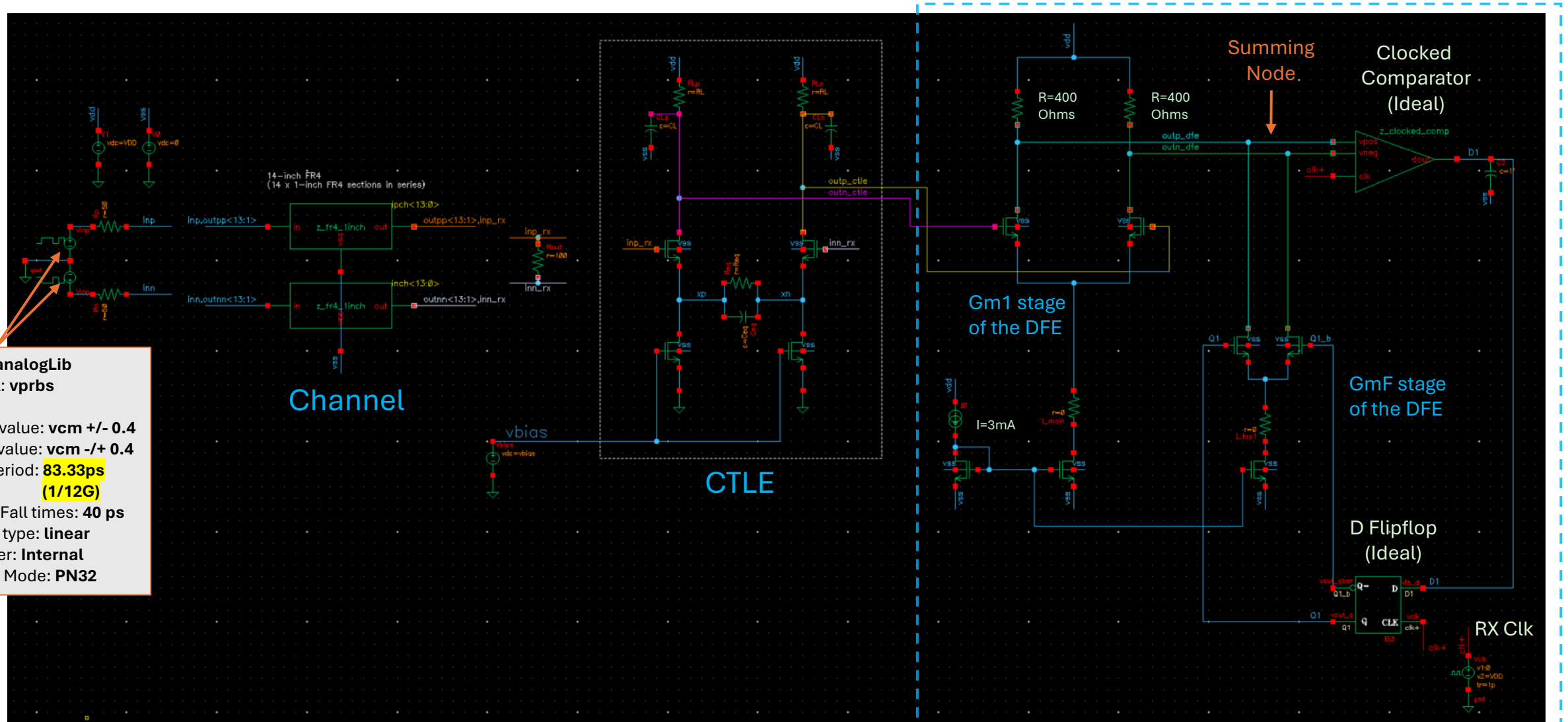
Rise/Fall times: 40 ps
Edge type: linear
Trigger: Internal
LFSR Mode: PN32




Testbench

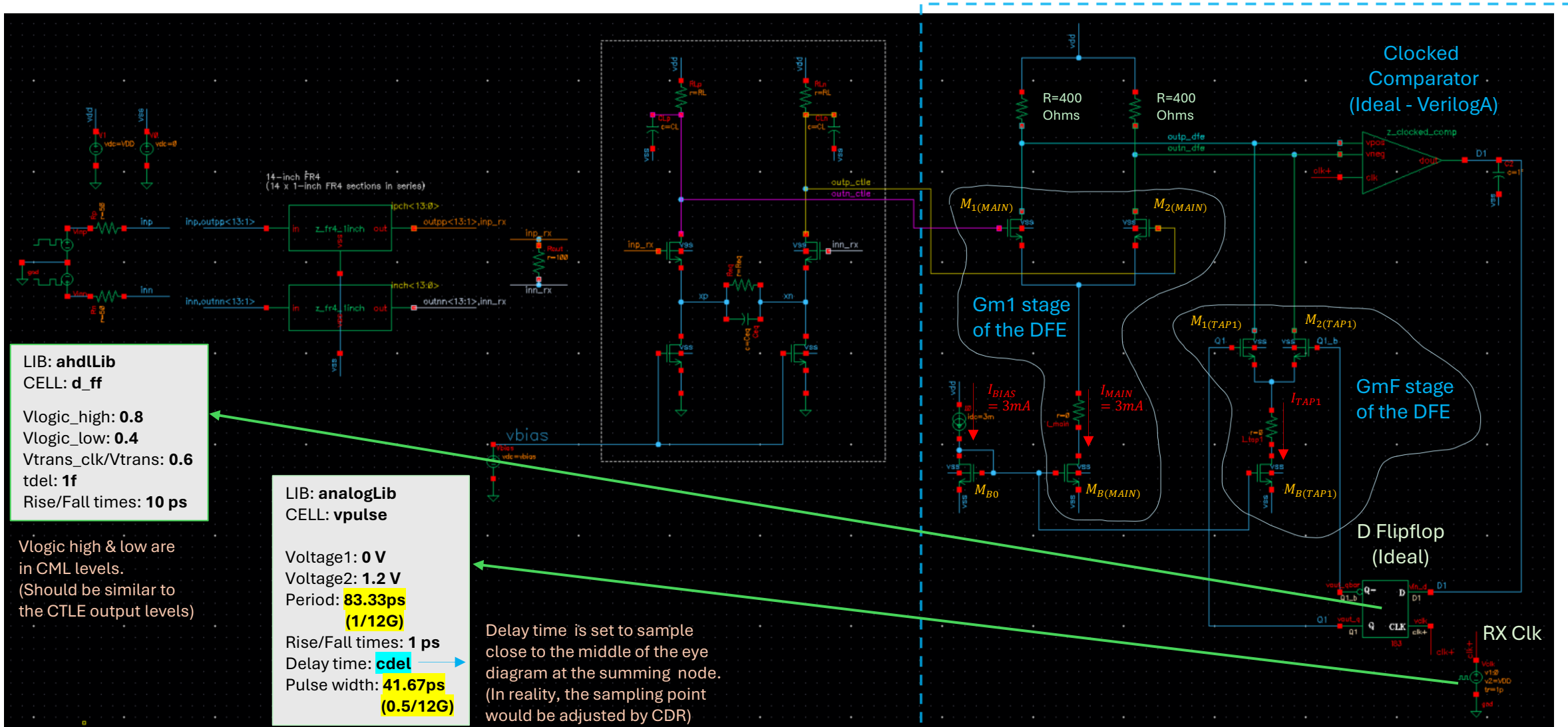

c) Eye Diagrams: Setup

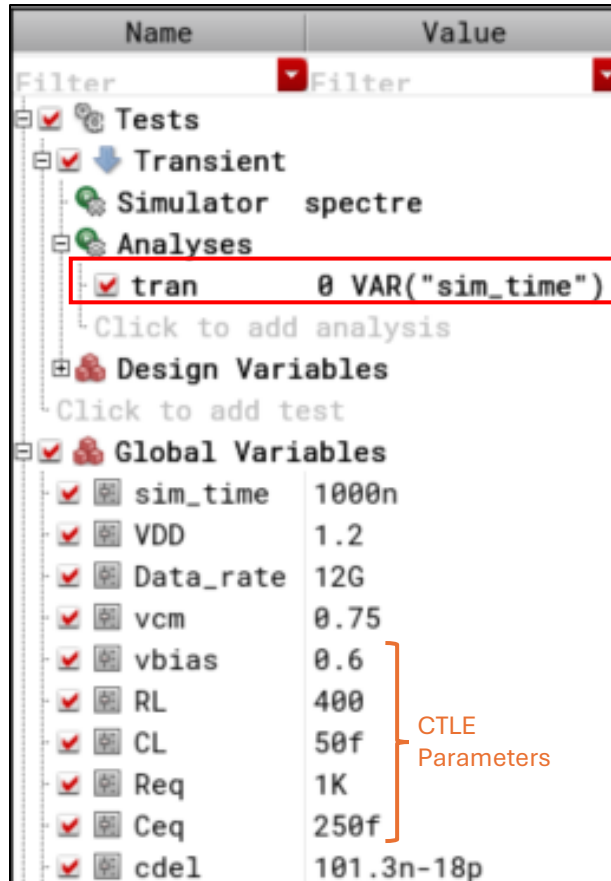

CTLE
Parameters

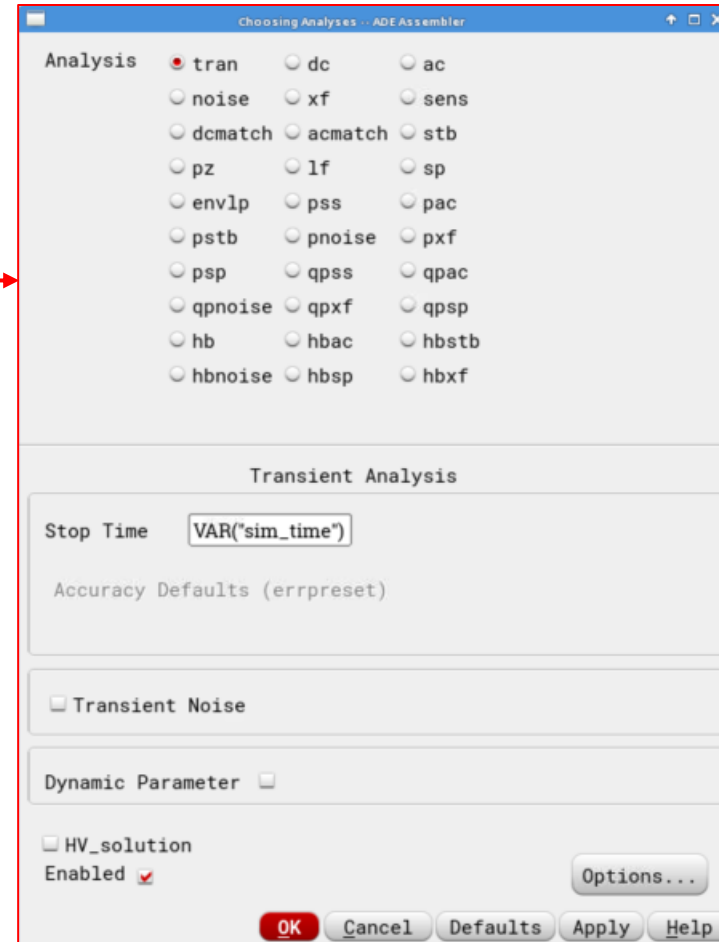

c) Eye Diagrams: Measurements


Name	Type	Details	EvalType
Filter	Filter	Filter	Filter
	signal	/vcm	point
	signal	/inp	point
	signal	/inn	point
	signal	/inp_rx	point
	signal	/inn_rx	point
	signal	/outp_ctle	point
	signal	/outn_ctle	point
	signal	/outp_dfe	point
	signal	/outn_dfe	point
	signal	/D1	point
	signal	/Q1	point
	signal	/Q1_b	point
	signal	/clk+	point
	signal	/clk-	point
*** PK2PK ***	expr		point
Vchin_pk2pk	expr	(VT("/inp") - VT("/inn"))	point
Vchout_pk2pk	expr	(VT("/inp_rx") - VT("/inn_rx"))	point
Vctleout_pk2pk	expr	(VT("/outp_ctle") - VT("/outn_ctle"))	point
Vdfeout_pk2pk	expr	(VT("/outp_dfe") - VT("/outn_dfe"))	point
*** EYE ***	expr		point
EYE_ch_out	expr	eyeDiagram(Vchout_pk2pk 5e-07 VAR("sim_time") (2 * (1 / VAR("Data_rate")))) ?autoCenter t)	point
EYE_ctle_out	expr	eyeDiagram(Vctleout_pk2pk 5e-07 VAR("sim_time") (2 * (1 / VAR("Data_rate")))) ?autoCenter t)	point
EYE_dfe_out	expr	eyeDiagram(Vdfeout_pk2pk 5e-07 VAR("sim_time") (2 * (1 / VAR("Data_rate")))) ?autoCenter t)	point
*** Currents ***	expr		point
/I_main/MINUS_I	signal	/I_main/MINUS	point
/I_tap1/MINUS_I	signal	/I_tap1/MINUS	point

Peak-to-Peak Values

Eye Diagrams

c) Eye Diagrams: Results (Eye Diagrams)

1) No Equalization

 

c) Eye Diagrams:


Results (Eye Diagrams)

$$I_{TAP1} = 5\% * I_{MAIN} = 150\mu A$$

$$W_{MB(TAP1)} = 5\% * W_{MB(MAIN)}$$

$$W_{M1,2(TAP1)} = 5\% * W_{M1,2(MAIN)}$$

2) DFE 1-tap Equalization: (tap1 = 5%)

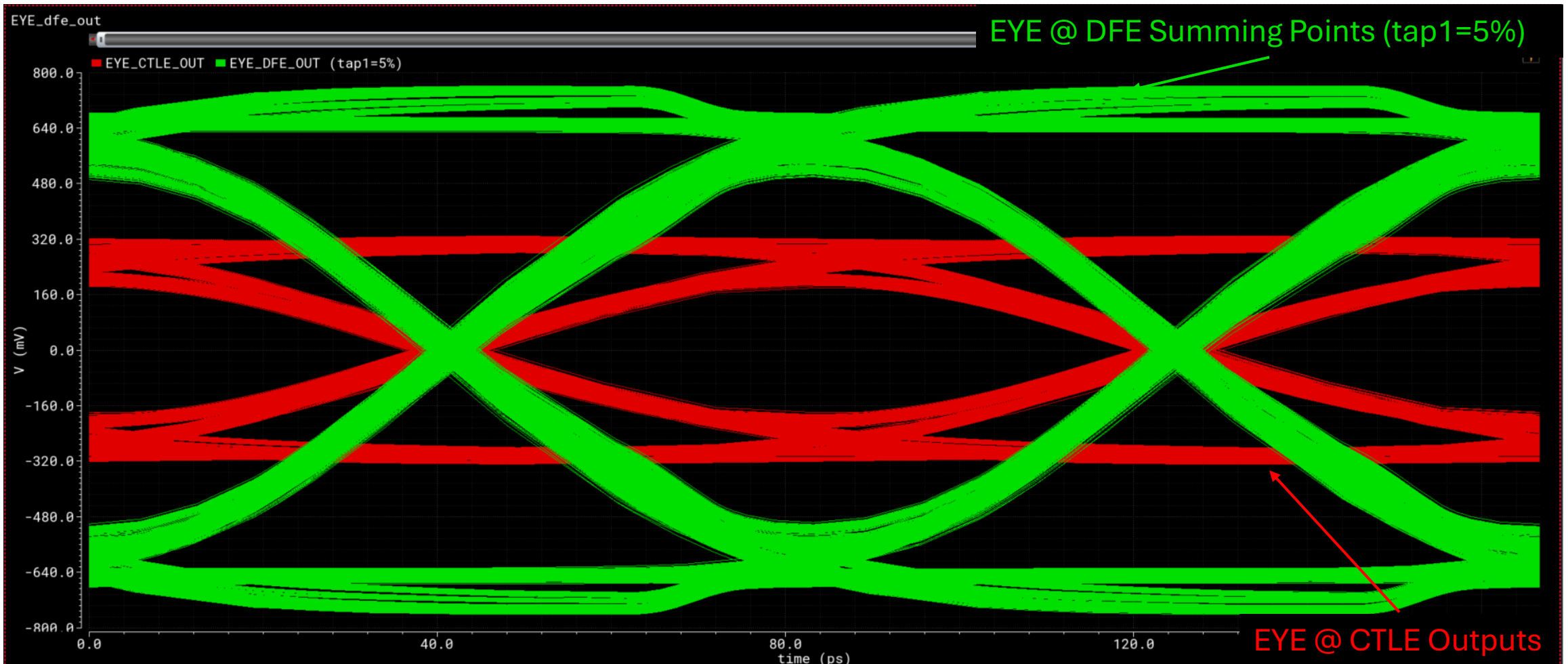

c) Eye Diagrams:


Results (Eye Diagrams)

$$I_{TAP1} = 10\% * I_{MAIN} = 300\mu A$$

$$W_{MB(TAP1)} = 10\% * W_{MB(MAIN)}$$

$$W_{M1,2(TAP1)} = 10\% * W_{M1,2(MAIN)}$$

3) DFE 1-tap Equalization: (tap1 = 10%)

 

c) Eye Diagrams:


Results (Eye Diagrams)

$$I_{TAP1} = 15\% * I_{MAIN} = 450\mu A$$

$$W_{MB(TAP1)} = 15\% * W_{MB(MAIN)}$$

$$W_{M1,2(TAP1)} = 15\% * W_{M1,2(MAIN)}$$

4) DFE 1-tap Equalization: (tap1 = 15%)

 

c) Eye Diagrams:


Results (Eye Diagrams)

$$I_{TAP1} = 30\% * I_{MAIN} = 900\mu A$$

$$W_{MB(TAP1)} = 30\% * W_{MB(MAIN)}$$

$$W_{M1,2(TAP1)} = 30\% * W_{M1,2(MAIN)}$$

5) DFE 1-tap Equalization: (tap1 = 30%)

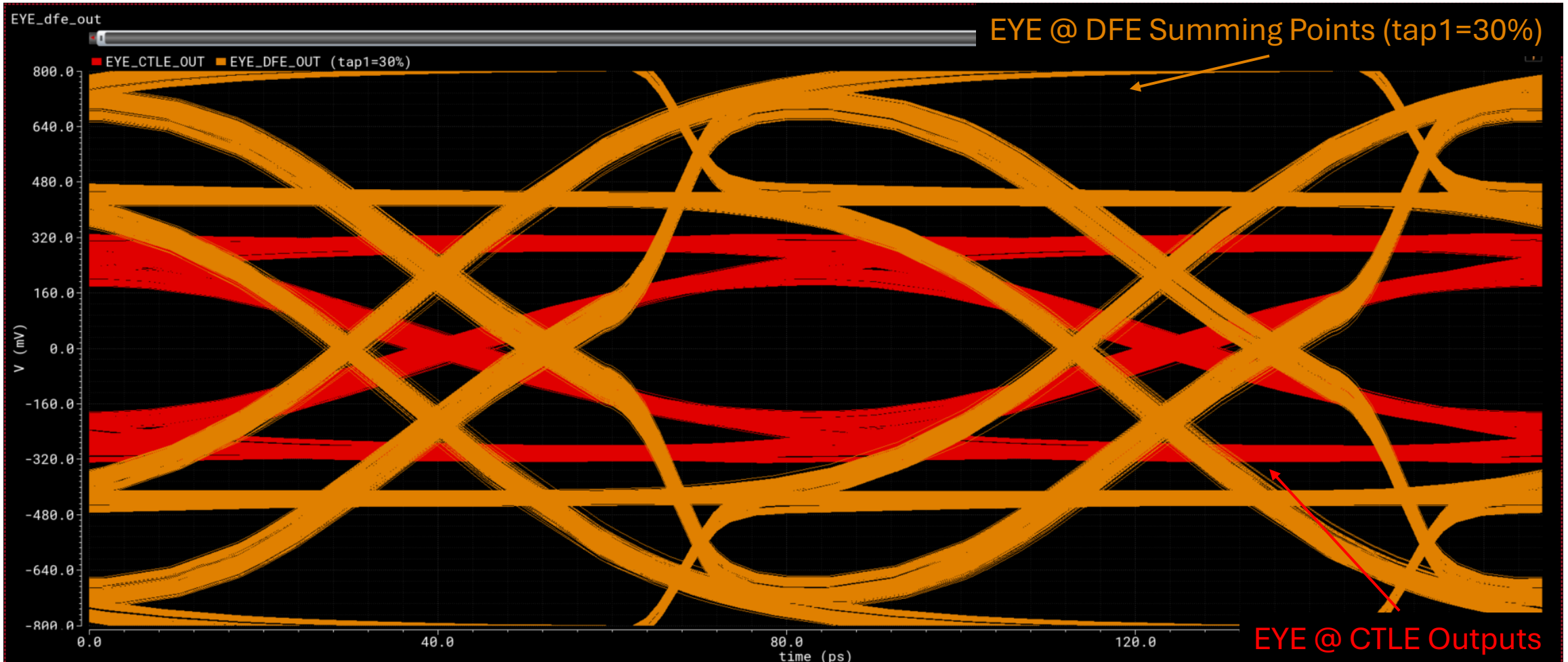

c) Eye Diagrams:

Results (Eye Diagrams)

	DFE Out Eye Measurements				
	No Equalization	tap1=5%	tap1=10%	tap1=15%	tap1=30%
Max Eye Height	0.891 V	0.996 V	1.065 V	1.037 V	0.796 V
Max Eye Width	73.22 ps	76.62 ps	72.49 ps	67.98 ps	54.13 ps
Eye S/N	6.182 dB	7.321 dB	8.043 dB	8.472 dB	4.962 dB
Pk2Pk Jitter	10.58 ps	7.20 ps	11.39 ps	15.99 ps	29.87 ps


➔ All the Eye measurement parameters improve as the tap current increases from 0 (no equalization) up to a certain point, then the Eye starts to shrink & the jitter increases. That's because the DFE improves the high-frequency components of the data at the expense of the low-frequency components of the data. *

(Check Waveforms in next Slide)

[*] Y. Li and F. Yuan, "Adaptive data-transition decision feedback equalizer for serial links," *2017 IEEE 60th International Midwest Symposium on Circuits and Systems (MWSCAS)*, Boston, MA, USA, 2017, pp. 1609-161

c) Eye Diagrams:

Results (Transient Waveforms)

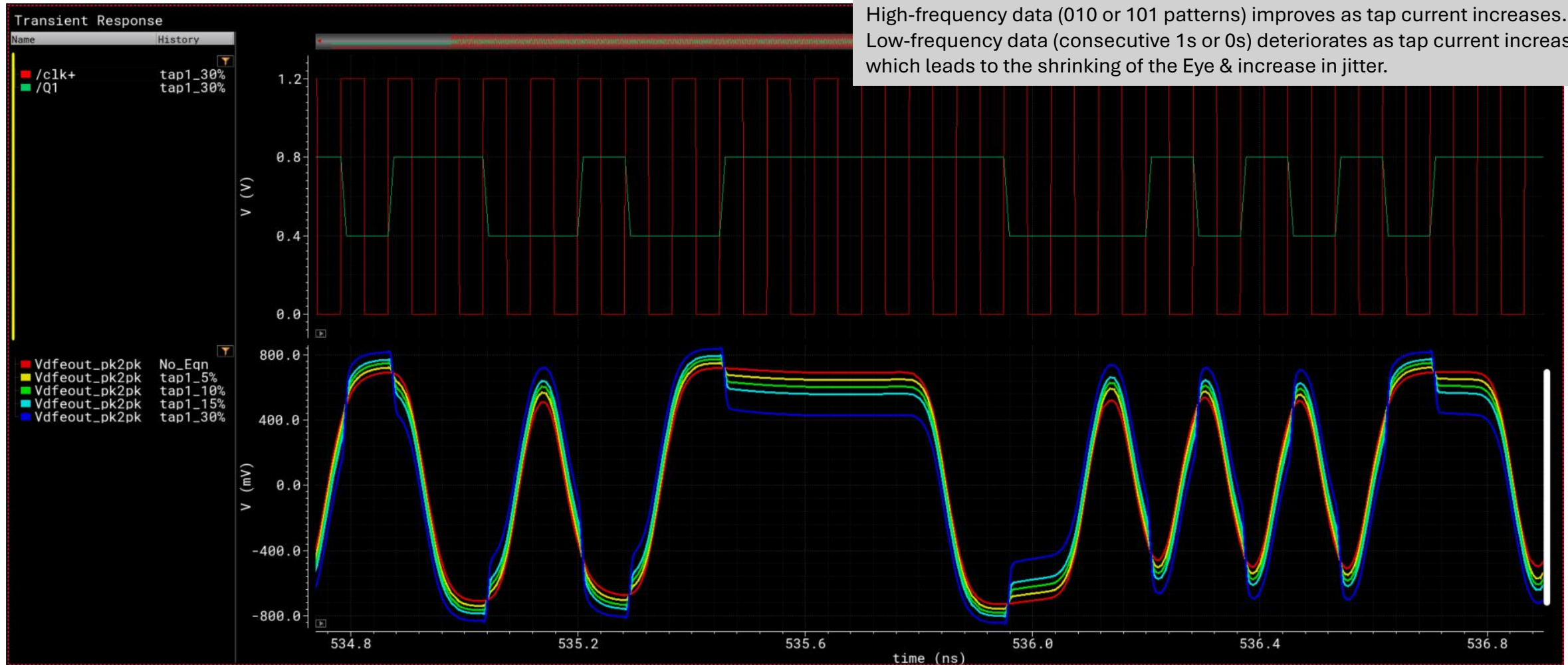


Final Results & Remarks

Final Results

→ Eye Diagram @ Channel Outputs

EYE @ Channel Outputs

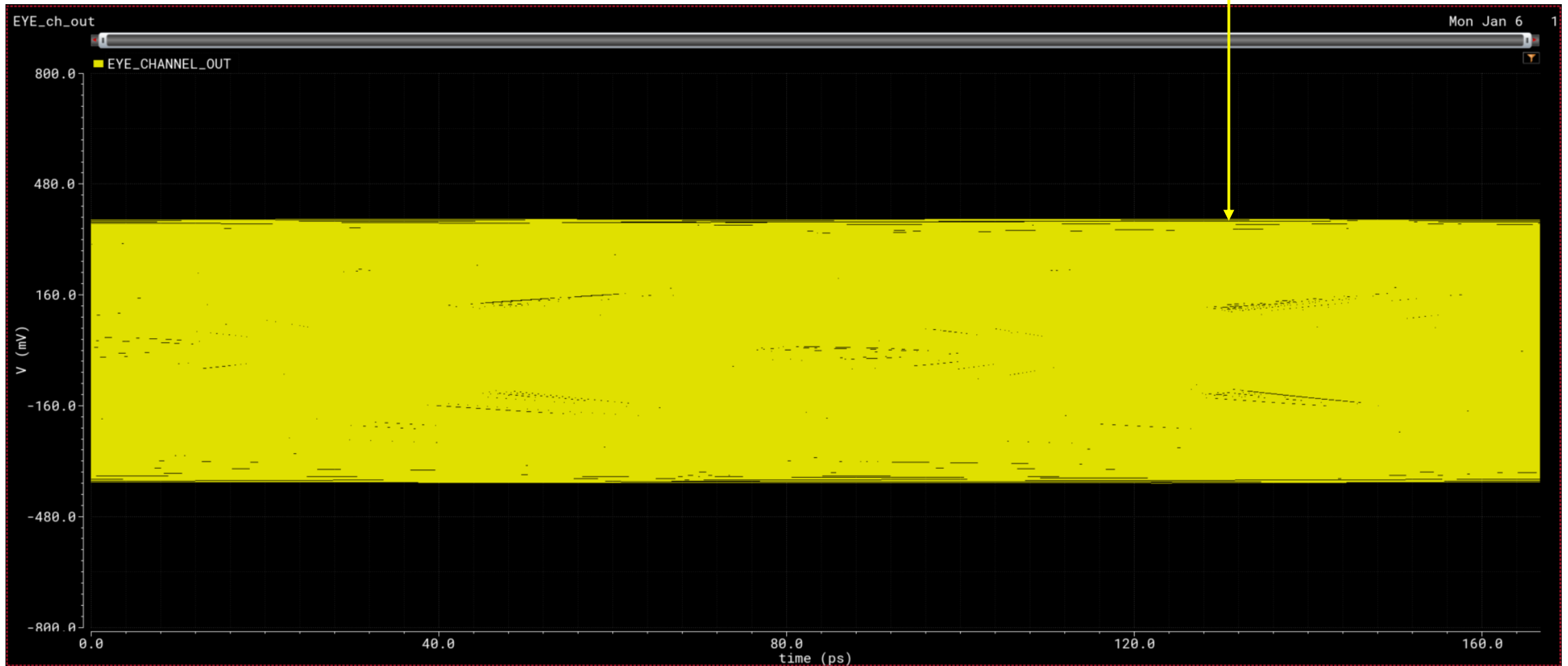


Final Results

→ Eye Diagram @ CTLE Outputs

EYE @ CTLE Outputs

EYE @ Channel Outputs

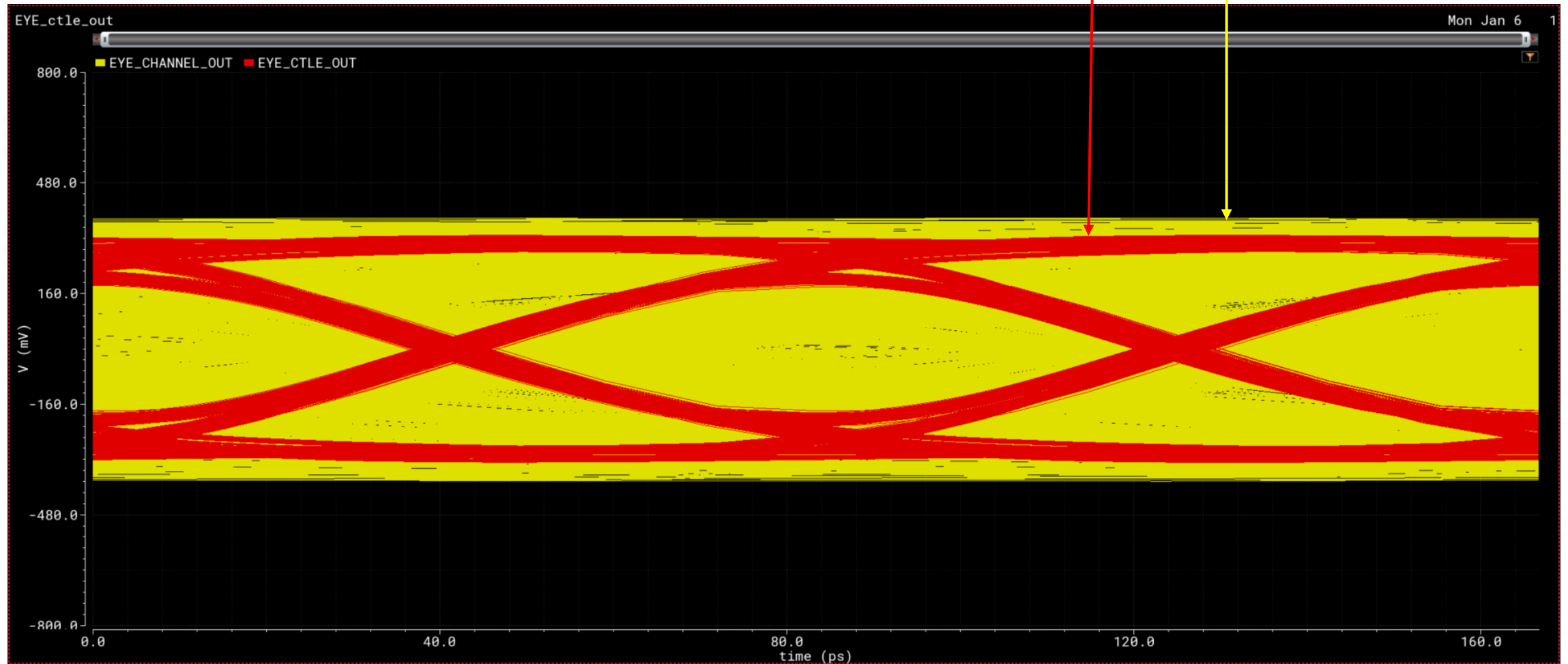


Final Results

→ Eye Diagram @ DFE Outputs

EYE @ DFE Summing Points (tap1=5%)

EYE @ CTLE Outputs

EYE @ Channel Outputs

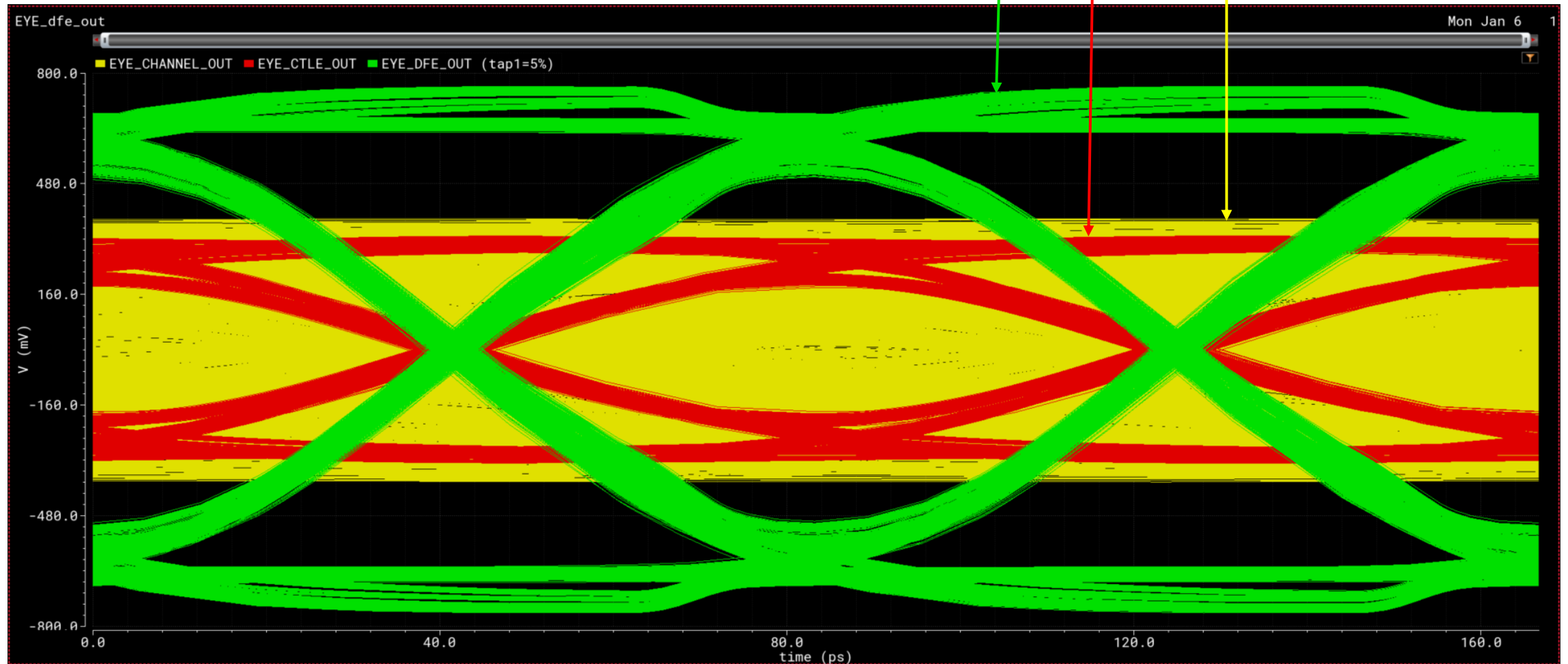

Final Results

➔ Eye Diagram Measurements:

	Eye Measurements	
	After CTLE	After DFE
Max Eye Height	359 mV	996 mV
Max Eye Width	73.23 ps	76.62 ps
Eye SNR	5.63 dB	7.32 dB
Pk2Pk Jitter	10.26 ps	7.20 ps

Final Remarks

- The system may not need to use DFE (or higher-tap DFE) if CTLE can give an enough eye opening.
- Future Work:
 1. **Current-steering** fliflops should be carefully designed for the feedback path of the DFE. ([Current-Steering FF lab](#))
 2. **Data-State DFE** can be used to improve high-freq data without affecting low-freq data. ([Paper](#))
 3. **Loop unrolling** technique can be used to improve timing margins at higher speeds. ([Lec Note](#))